

Series and Parallel Circuits

Question Paper

| | |
|------------------|-------------------------------------|
| Level | GCSE (9-1) |
| Subject | Combined Science: Trilogy - Physics |
| Exam Board | AQA |
| Topic | 6.2 Electricity |
| Sub-Topic | Series and Parallel Circuits |
| Difficulty Level | Bronze Level |
| Booklet | Question Paper |

Time Allowed: 17 minutes

Score: /17

Percentage: /100

Grade Boundaries:


Q1.(a) Draw **one** line from each circuit symbol to its correct name.

Circuit symbol


Name



Diode

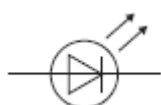

Light-dependent resistor (LDR)

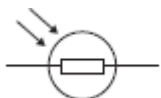

Lamp

Light-emitting diode (LED)

(3)

(b) **Figure 1** shows three circuits.

The resistors in the circuits are identical.




Each of the cells has a potential difference of 1.5 volts.

Figure 1

Circuit 1

Circuit 2

Circuit 3

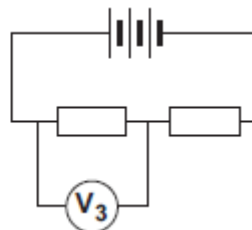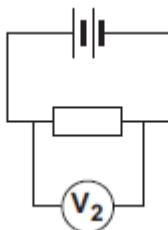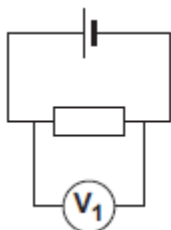

(i) Use the correct answer from the box to complete the sentence.

half

twice

the same as

The resistance of **circuit 1** is the resistance of **circuit 3**.

(1)

(ii) Calculate the reading on voltmeter V_2 .

.....

Voltmeter reading $V_2 = \dots\dots\dots$ V

(1)

(iii) Which voltmeter, V_1 , V_2 or V_3 , will give the lowest reading?

Draw a ring around the correct answer.

V_1

V_2


V_3

(1)

(c) A student wanted to find out how the number of resistors affects the current in a series circuit.

Figure 2 shows the circuit used by the student.

Figure 2

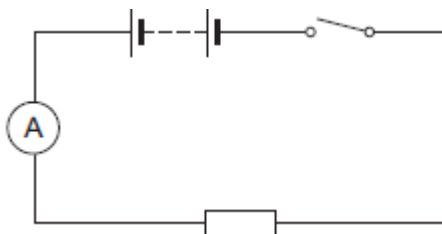


The student started with one resistor and then added more identical resistors to the circuit.

Each time a resistor was added, the student closed the switch and took the ammeter reading.

The student used a total of 4 resistors.

Figure 3 shows three of the results obtained by the student.

Figure 3

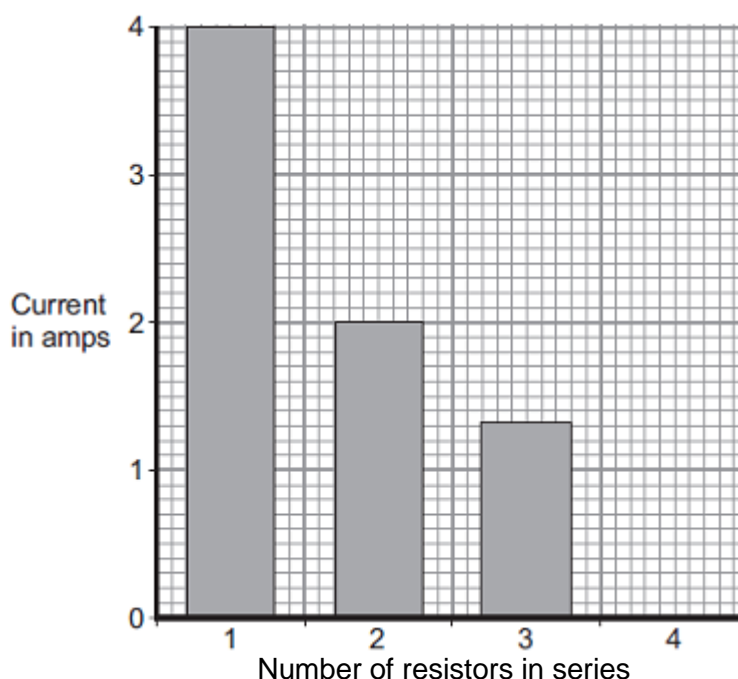

- (i) To get valid results, the student kept one variable the same throughout the experiment.

Which variable did the student keep the same?

.....

(1)

- (ii) The bar chart in **Figure 3** is not complete. The result using 4 resistors is not shown.

Complete the bar chart to show the current in the circuit when 4 resistors were used.

(2)

- (iii) What conclusion should the student make from the bar chart?

.....


.....

(1)

(Total 10 marks)

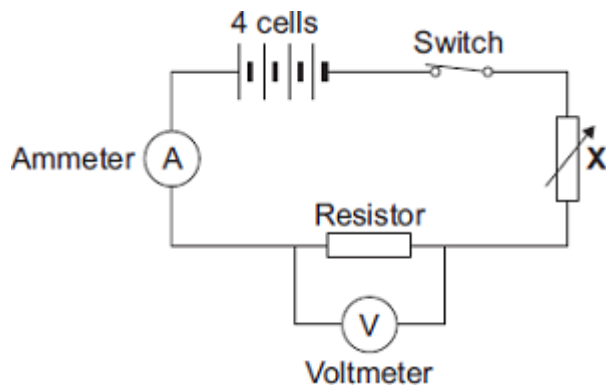Q2.(a) The diagram shows the circuit that a student used to investigate how the current through a

resistor depends on the potential difference across the resistor.



- (i) Each cell provides a potential difference of 1.5 volts.

What is the total potential difference provided by the four cells in the circuit?

.....

Total potential difference = volts

(1)

- (ii) The student uses the component labelled **X** to change the potential difference across the resistor.

What is component **X**?

Draw a ring around your answer.

light-dependent resistor

thermistor

variable resistor


(1)

- (iii) Name a component connected in parallel with the resistor.

.....

(1)

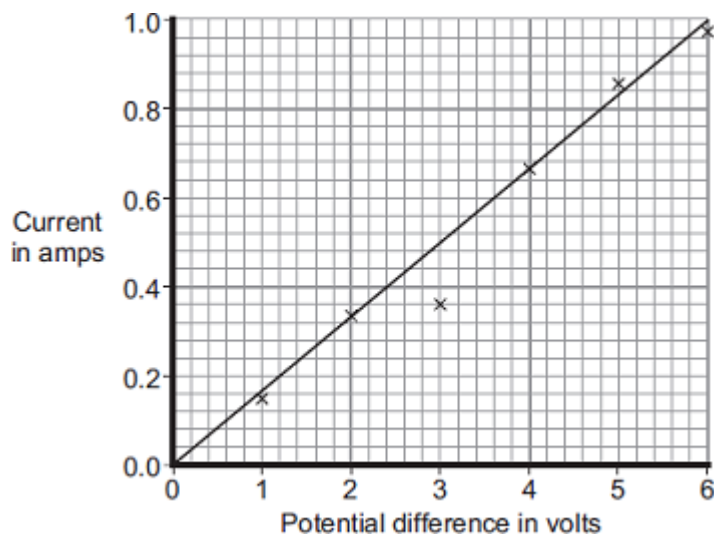- (b) The results obtained by the student have been plotted on a graph.



- (i) One of the results is anomalous.

Draw a ring around the anomalous result.

(1)

- (ii) Which **one** of the following is the most likely cause of the anomalous result?

Put a tick (✓) in the box next to your answer.

The student misread the ammeter.

☐

The resistance of the resistor changed.

☐

The voltmeter had a zero error.

☐

(1)

- (iii) What was the interval between the potential difference values obtained by the student?

.....

(1)

- (c) Describe the relationship between the potential difference across the resistor and the current through the resistor.

.....

.....

(1)
(Total 7 marks)