

Current Potential Diff and Resistance

Mark Scheme 1

Level	GCSE (9-1)
Subject	Combined Science: Trilogy - Physics
Exam Board	AQA
Topic	6.2 Electricity
Sub-Topic	Current Potential Diff and Resistance
Difficulty Level	Gold Level
Booklet	Mark Scheme 1

Time Allowed: 59 minutes

Score: /57

Percentage: /100

Grade Boundaries:

M1.(a)	$1\,950 / 2\,500 \times 100$	1
	78 (%)	1
(b)	expected mass of aluminium	
	$1950 \times 54 / 102$	1
	= 1032.35	1
	mass not collected	
	$1032.35 - 1\,000$	
	= 32.4	
	<i>allow 32.4 with no working shown for 3 marks</i>	1
	<i>incorrect number of sig. figs max 2 marks</i>	
(c)	because oxygen is formed at the anode	1
	which reacts with the carbon anode to produce carbon dioxide	1
	and wears it away	1

(d) power = $1.5 \times 10^5 \times 4$ 1

= 6.0×10^5 W 1

24 hours = $24 \times 60 \times 60 = 8.64 \times 10^4$ seconds 1

energy transferred = $6.0 \times 10^5 \times 8.64 \times 10^4$
allow ecf from power calculation 1

= 5.184×10^{10}
allow 5.184×10^{10} with no working for 5 marks 1


(e) 3 moles of electrons are needed to produce 27 g or 0.027 kg aluminium 1

so moles of electrons to produce 1 000 kg = $1\,000 / 0.027 \times 3$ 1

= 111 000
allow 111 000 with no working shown for 3 marks
incorrect no. of sig. figs max 2 marks 1

[16]

M2.(a)

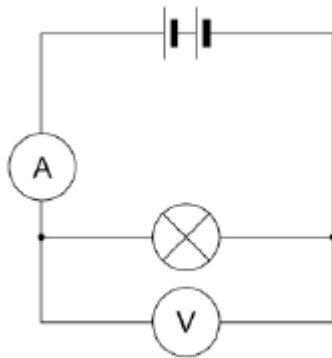

ammeter connected in series

1

voltmeter connected in parallel

1

measure the potential difference across the lamp at known current

1

calculate resistance from measured values using $V = IR$

1

- (b) for ohmic conductors the current is directly proportional to the potential difference applied across it

1

this graph is curved so it is not an ohmic conductor

1

- (c) diode

1

because it has a high resistance with negative potential differences

1

and a low resistance for positive potential differences.

1

allow answers in terms of current

(d) tangent to the curve drawn at 2.3 V

1

correct reading of Δy and Δx from graph

1

either

substitution of values into $V = IR$ (1)

1

value of R calculated (1)

accept values in the range 0.50 to 0.65

1

or

calculation of gradient (1)

allow ecf from incorrect readings of Δy and Δx

calculation of $R = 1 / \text{gradient}$ (1)

accept values in the range 0.50 to 0.65

[13]

M3.(a) (i)




1

(ii) 360

allow 1 mark for correct substitution, ie $9 = 0.025 \times R$

2

(iii) sketch graph of correct shape, ie

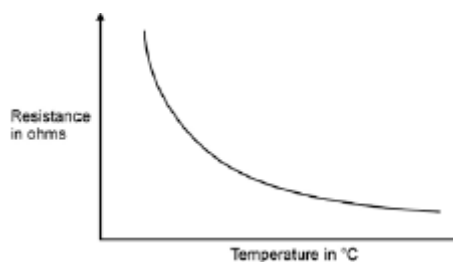

1

(iv) An automatic circuit to switch a heating system on and off.

1

(b) so ammeter reduces / affects current as little as possible

accept so does not reduce / change the current (it is measuring)

accurate reading is insufficient

not change the resistance is insufficient

1

(c) gives a common understanding

accept is easier to share results

accept can compare results

do not need to be converted is insufficient

prevent errors is insufficient

1

(d) replace Bunsen (and water) with a lamp

accept any way of changing light level

1

replace thermometer with light sensor

accept any way of measuring a change in light level

datalogger alone is insufficient

1

[9]

M4.(a) 35

an answer with more than 2 sig figs that rounds to 35 gains 2 marks

allow 2 marks for correct method, ie $\frac{230}{6.5}$

allow 1 mark for $I = 6.5$ (A) or $R = \frac{230}{26}$

an answer 8.8 gains 2 marks

an answer with more than 2 sig figs that rounds to 8.8 gains 1 mark

3

- (b) (maximum) current exceeds maximum safe current for a 2.5 mm² wire
accept power exceeds maximum safe power for a 2.5 mm² wire

or(maximum) current exceeds 20 (A)

(maximum) current = 26 (A) is insufficient

1

a 2.5 mm² wire would overheat / melt

accept socket for wire

*do **not** accept plug for wire*

1

- (c) a.c. is constantly changing direction

accept a.c. flows in two directions

accept a.c. changes direction

a.c. travels in different directions is insufficient

1

d.c. flows in one direction only

1


[7]

M5.(a) (i) symbol for a diode



1

symbol for a variable resistor

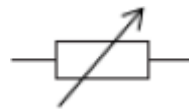

1

(ii) voltmeter is in series **or** voltmeter is not in parallel

1

ammeter is in parallel **or** ammeter is not in series

accept an answer in terms of how the circuit should be corrected

voltmeter and ammeter are wrong way around is insufficient

1

(b) (i) 0.2 (V)

accept any value between 0.20 and 0.21 inclusive

1

(ii) 37.5

allow 1 mark for $I = 0.008$

or

allow 2 marks for correct substitution, ie $0.3 = 0.008 \times R$

or

*allow 1 mark for a correct substitution using $I = 0.8$ **or** $I = 0.08$ **or** $I = 0.009$*

or

*allow 2 marks for answers of 0.375 **or** 3.75 **or** 33(.3)*

3

(c) (i) 25

allow 1 mark for obtaining period = 0.04(s)

2

(ii) diode has large resistance in reverse / one direction

1

so stops current flow in that / one direction

allow diodes only let current flow one way / direction

allow 1 mark for the diode has half-rectified the (a.c. power) supply

1

[12]