

# Series and Parallel Circuits

## Mark Scheme

<b>Level</b>	GCSE (9-1)
<b>Subject</b>	Combined Science: Trilogy - Physics
<b>Exam Board</b>	AQA
<b>Topic</b>	6.2 Electricity
<b>Sub-Topic</b>	Series and Parallel Circuits
<b>Difficulty Level</b>	Silver Level
<b>Booklet</b>	Mark Scheme

**Time Allowed:** 9 minutes

**Score:** /9

**Percentage:** /100

**Grade Boundaries:**

- M1.(a) 0.093 A 1
- (b) 0.093 A 1
- (c) (increasing the resistance) decreases the current 1
- therefore (the lamp will be) dimmer 1
- (d) potential difference = current  $\times$  resistance  
*accept correct rearrangement with R as subject* 1
- (e)  $3.3 = 0.15 \times R$  1
- $R = 3.3 / 0.15 (\Omega)$  1
- $R = 22 (\Omega)$  1
- allow 22 ( $\Omega$ ) without working shown for 3 marks*
- (f) line drawn from the origin with a decreasing gradient. 1

## Save My Exams! – The Home of Revision

For more awesome GCSE and A level resources, visit us at [www.savemyexams.co.uk/](http://www.savemyexams.co.uk/)