

# Current Potential Diff and Resistance

## Mark Scheme 1

<b>Level</b>	GCSE (9-1)
<b>Subject</b>	Combined Science: Trilogy - Physics
<b>Exam Board</b>	AQA
<b>Topic</b>	6.2 Electricity
<b>Sub-Topic</b>	Current Potential Diff and Resistance
<b>Difficulty Level</b>	Bronze Level
<b>Booklet</b>	Mark Scheme 1

**Time Allowed:** 56 minutes

**Score:** /56

**Percentage:** /100

**Grade Boundaries:**

**M1.(a)** (i) any **six** from:

- switch on
- read both ammeter and voltmeter  
*allow read the meters*
- adjust variable resistor to change the current
- take further readings
- draw graph
- (of) V against I  
*allow take mean*
- $R = V / I$   
*allow take the gradient of the graph*

6

(ii) resistor would get hot if current left on

1

so its resistance would increase

1

(iii) 12 (V)

*0.75 × 16 gains 1 mark*

2

(iv) 15 (Ω)

1

16 is nearer to that value than any other

1

(b) if current is above 5 A / value of fuse

1

fuse melts

allow blows / breaks  
do **not** accept exploded


1

breaks circuit

1

[15]

M2.(a)

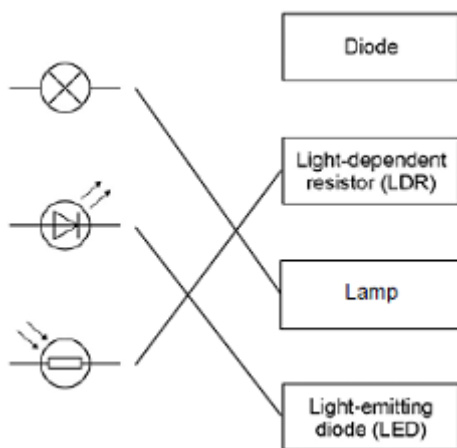

allow 1 mark for each correct line if more than one line is drawn from any symbol then all of those lines are wrong

3

(b) (i) half

1

(ii) 3(V)

1

(iii)  $V_1$

1

(c) (i) potential difference / voltage of the power supply  
accept the power supply  
accept the voltage / volts  
accept number of cells / batteries  
accept (same) cells / batteries  
do not accept same ammeter / switch / wires

1

(ii) bar drawn – height 1.(00)A  
ignore width of bar  
allow 1 mark for bar shorter than 3<sup>rd</sup> bar

2

(iii) as the number of resistors increases the current decreases

1

[10]

**M3.(a)** 25( $\Omega$ )

1

(b) (i) 2(V)

*allow 1 mark for showing a correct method, ie 6 / 3*

2

(ii) equal to

1

[4]

**M4.(a)** (i) 50 (Hz)

1

(ii) 2760 (W)

1

(b) 12

*allow 1 mark for correct substitution, ie 2400/200*

**or**

*allow 1 mark for 2760/230 provided no subsequent step shown*

2

amps

1

- (c) the charge is directly proportional to the time switched on for  
*accept for 1 mark the longer time (to boil), the greater amount of charge*  
*or positive correlation*  
*or they are proportional*

2

[7]

M5. (a) (i) 15

1

- (ii) 4.5 or their (a)(i)  $\times 0.3$  correctly calculated  
*allow 1 mark for correct substitution, ie  $0.3 \times 15$ /their (a)(i), provided no subsequent step*

2

- (ii) decrease

1

(b) Y

*accept any correct indication*  
*reason only scores if Y is chosen*  
*accept voltage for p.d.*

1

(only one that) shows a direct current / p.d.

**or**

a battery / cell gives a direct current

*accept both X and Z are a.c.*

**or**

a battery/cell gives a constant current/p.d.


*accept it's a constant current/p.d.*

*it is not changing is insufficient*

1

[6]

M6. (a) (i) correct symbol ringed

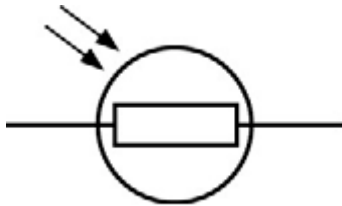

1

(ii) accept any suggestion that would change light intensity, eg:

- torch on or off  
*accept power of torch*  
*do **not** accept watts / wattage of torch*
- distance between torch and LDR
- lights in room on or off
- shadow over the LDR

1

(b) resistance decreases

1

from  $600\text{ k}\Omega$  to  $200\text{ k}\Omega$   
*accept by  $400\text{ k}\Omega$*

1

(c) (i) no numbers for light intensity  
**or**  
light intensity is categoric / a description / not continuous  
*not enough results is insufficient*

1

(ii) YES

*mark is for the reason*

both show that resistance increases with decreasing (light) intensity /  
brightness

*accept they both get the same results / pattern*

1

(d) A circuit that automatically switches outside lights on when it gets dark.

1

[7]

**M7.** (a) (i) 6

1

(ii) variable resistor

1

(iii) voltmeter

1

(b) (i) point at 3 V ringed

1

(ii) The student misread the ammeter.

1

(iii) 1 (volt)

*accept every volt*

1

- (c) as one increases so does the other ~~or~~ directly proportional ~~or~~ positive correlation  
*accept a numerical description, eg when one doubles the other also doubles*

1

[7]